

**AEC-II PROJECT REPORT**

9) Design and implement single phase Half-bridge Sinusoidal PWM inverter using MOSFET subject to following conditions:


1.  $V_{out}=9V$ , 50Hz,  $F_s=18kHz$ . Assume the load to be the secondary terminals of 9-0-9 transformer ( $I_L=120mA$  at the primary).
2. Design the PWM circuit (using 555 timer) to drive the above converter.

**TEAM:**


<u>NAME</u>	<u>USN</u>
<b>Rithesh</b>	<b>NNM22EC133</b>
<b>Rhith Shettigar</b>	<b>NNM22EC135</b>
<b>S Pancham Pai</b>	<b>NNM22EC136</b>
<b>Sai Janani</b>	<b>NNM22EC140</b>
<b>Salman Farish</b>	<b>NNM22EC141</b>
<b>Sammedh S Jain</b>	<b>NNM22EC142</b>

Date of submission: 19-04-2024

## CIRCUIT DIAGRAM:

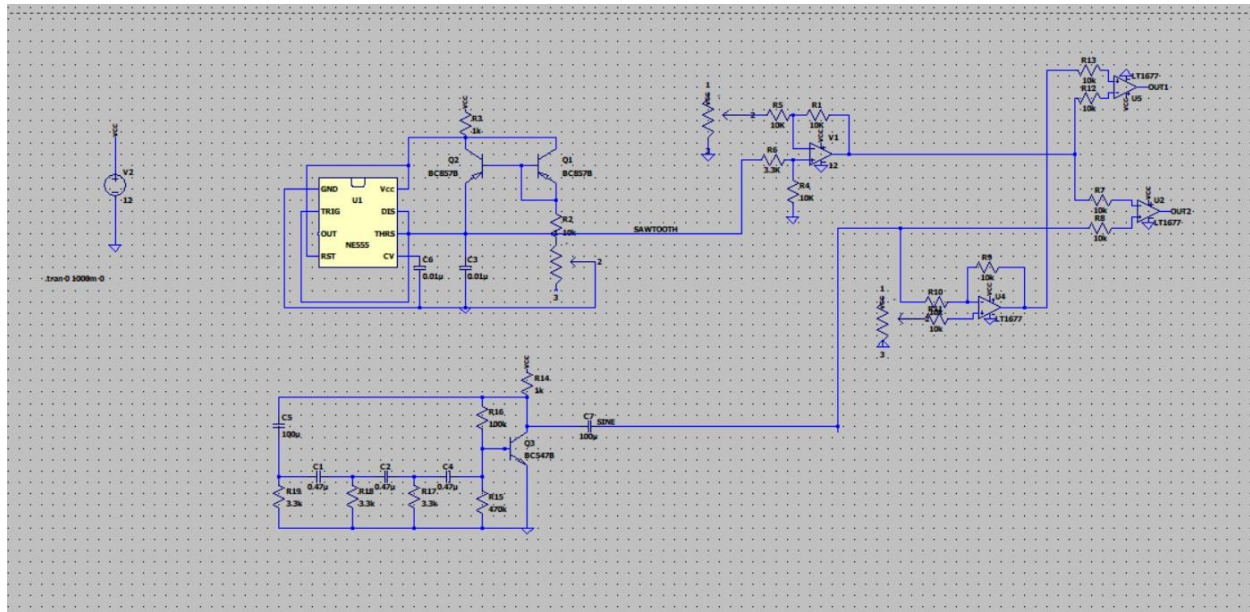

PWM Circuit

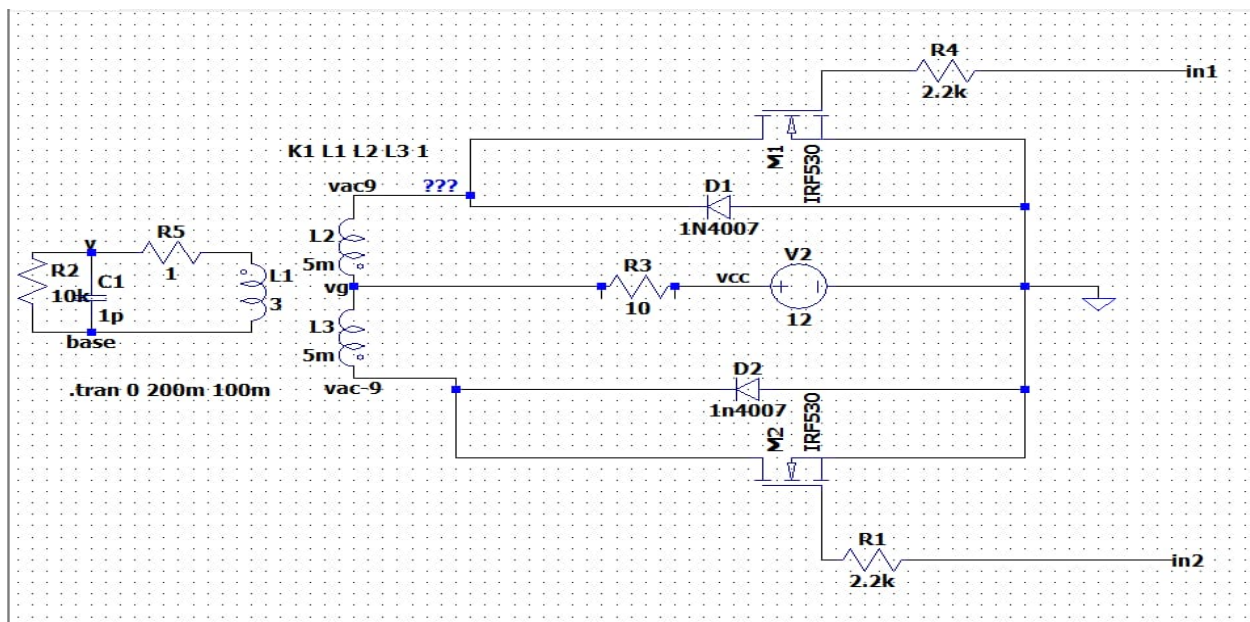

Inverter Circuit

## **CIRCUIT DESIGN:**

### **SPECIFICATIONS:**

- **RC Phase shift:**

In RC phase shift oscillator, sine wave is generated.

$$\text{Frequency of circuit (sine)} = f = \frac{1}{(2\pi RC\sqrt{2N})}$$

Where, N=No. of RC Pairs

R=resistor value

C=capacitor value

To obtain 50Hz,

Assume C=0.47μF

$$50 = \frac{1}{2\pi R(0.47\mu)\sqrt{2N}}$$

$$R = \frac{1}{(2\pi 50 \cdot 0.47\mu\sqrt{2})}$$

$$R = 2.764k\Omega$$

But due to the tolerance in the components and by applying the concept of trial and error we get, 'R=2.2kΩ' (Practically).

- **Sawtooth using 555 timer:**

$$f \approx \frac{3}{RC}$$

To obtain f=18kHz and C=0.01μF

$$R \approx \frac{3}{f_c}$$

$$R \approx \frac{3}{18k \cdot 0.01\mu} = 16.66k\Omega$$

Frequency was changing due to the cascading of circuits. So we connected (10k+10k(pot)) = R, to change the frequency as required.

$$R=10k + 10k(\text{potentiometer})$$

- **Difference Amplifier:**

$$V_{out} = \left[ 1 + \frac{R_f}{R_1} \right] \left[ \frac{R_3 V_{in1}}{R_2 + R_3} + \frac{R_2 V_{in2}}{R_2 + R_3} \right] - \frac{R_f}{R_1} V_{in2}$$

To obtain gain of 1.5 for  $V_{in1}$ :

$$V_{out} = 1.5V_{in1} - V_{in2}$$

$$\frac{R_f}{R_1} = 1$$

$$R_f = R_1$$

$$(1+1) \left( \frac{V_{in1} R_3}{R_2 + R_3} \right) = 1.5 V_{in1}$$

$$2R_3 = 1.5R_2 + 1.5R_3$$

$$0.5R_3 = 1.5R_2$$

$$R_3 = 3R_2$$

Assume,

$$R_1=10k\Omega, R_f=10k\Omega, R_3=12k\Omega$$

$$R_2 = \frac{R_3}{3} = 3.33k\Omega$$

- **Inverting Amplifier:**

**Assume  $R_f=R_1=R_2=10k\Omega$**

$$V_{out} = - \frac{R_f}{R_1} V_{in1}$$

$$V_{out} = - V_{in1}$$


- Using Op-amp as an inverting amplifier.
- To obtain inverted sine wave of same frequency and amplitude.

**EXPECTED RESULT:**

**The circuit should must be able to produce:**


- 18kHz frequency modulated pulse from PWM
- 9V, 50Hz input to the secondary terminals of a 9-0-9 transformer.

## HARDWARE CIRCUIT:

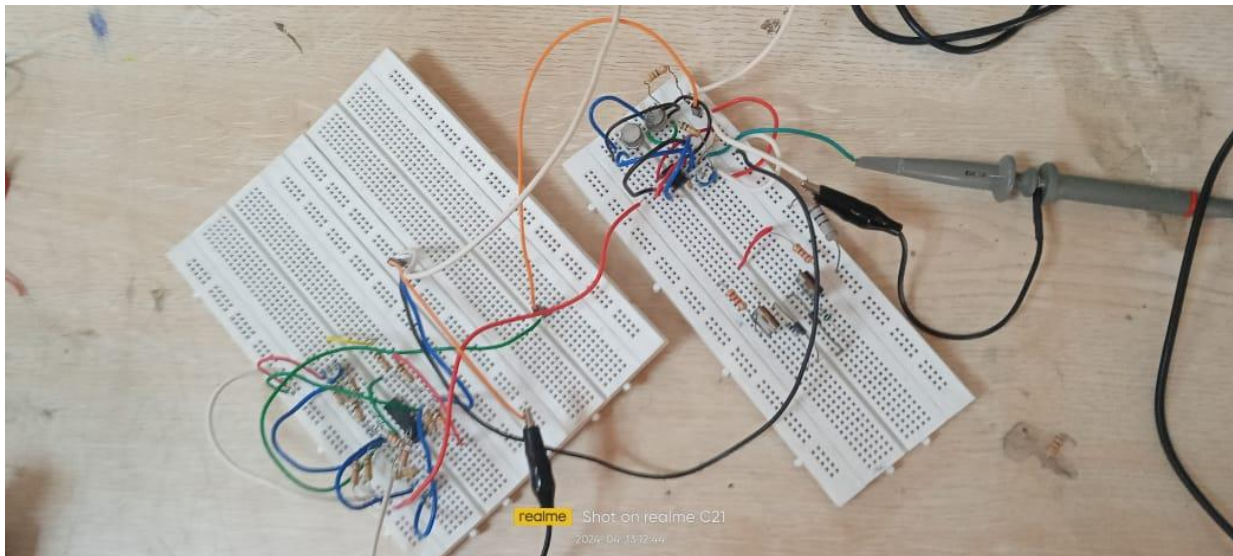


## SIMULATION RESULTS:


### Inverting Amplifier:

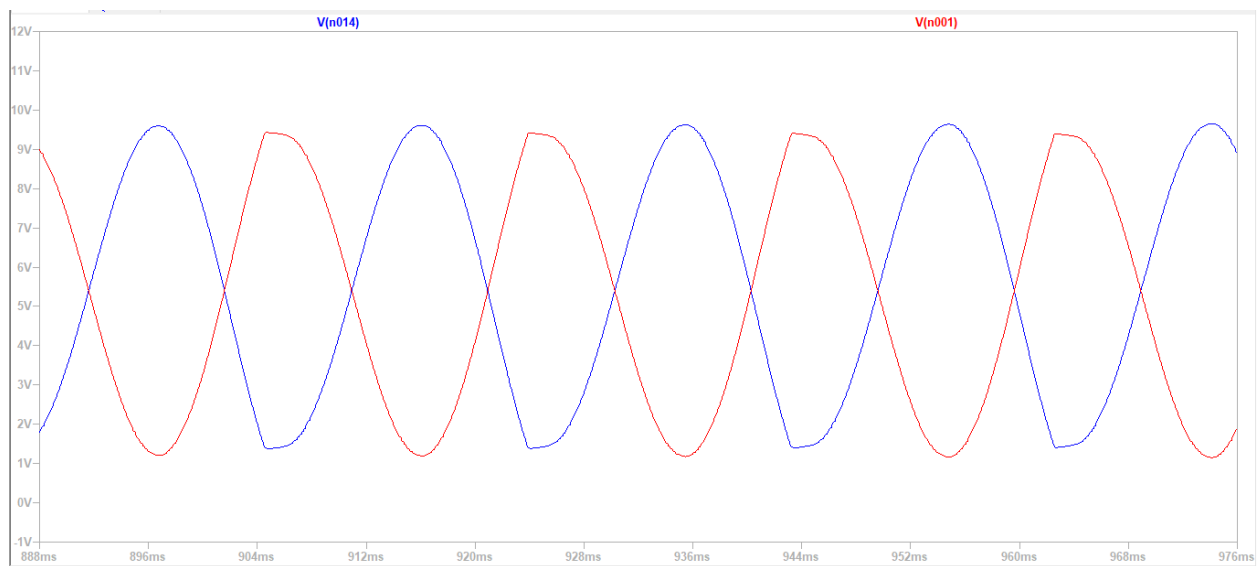


## Sine wave:

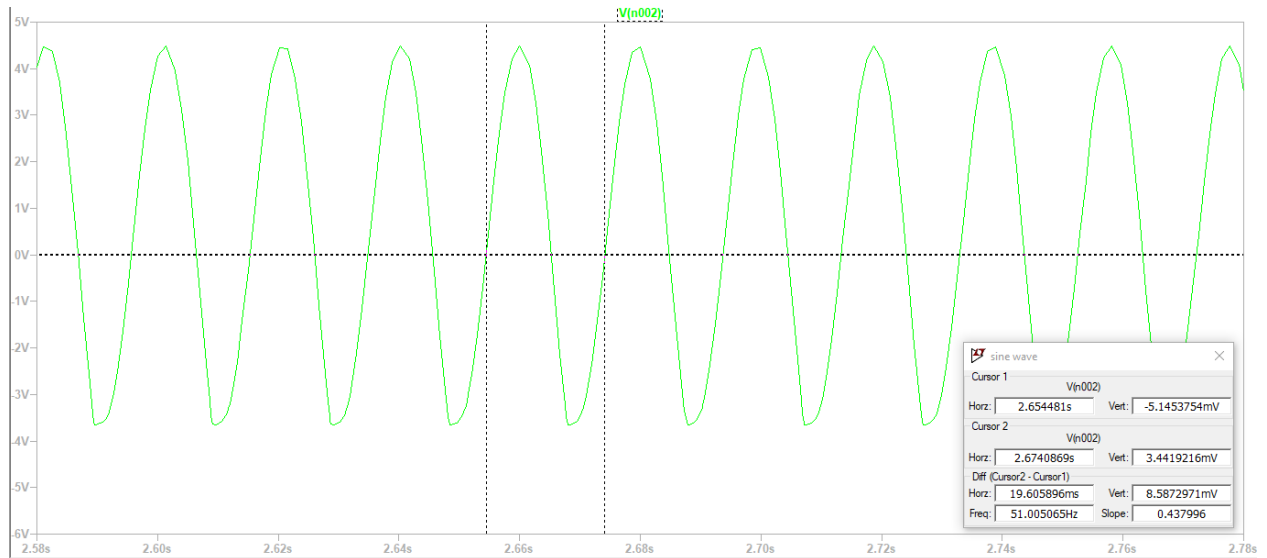

## Sawtooth:

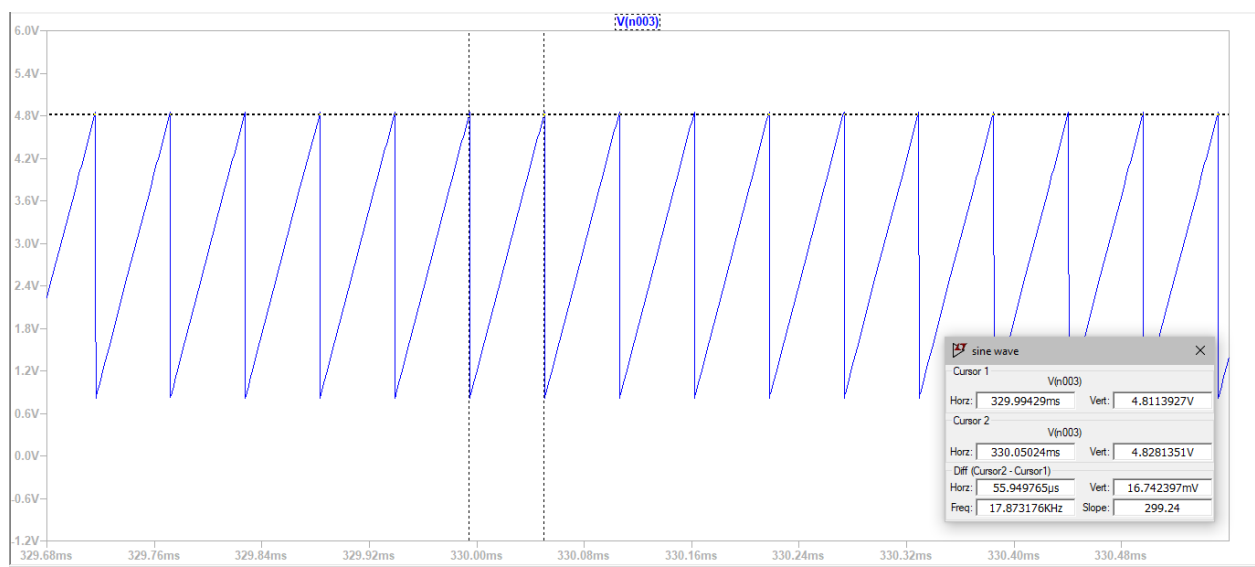


## Comparator:

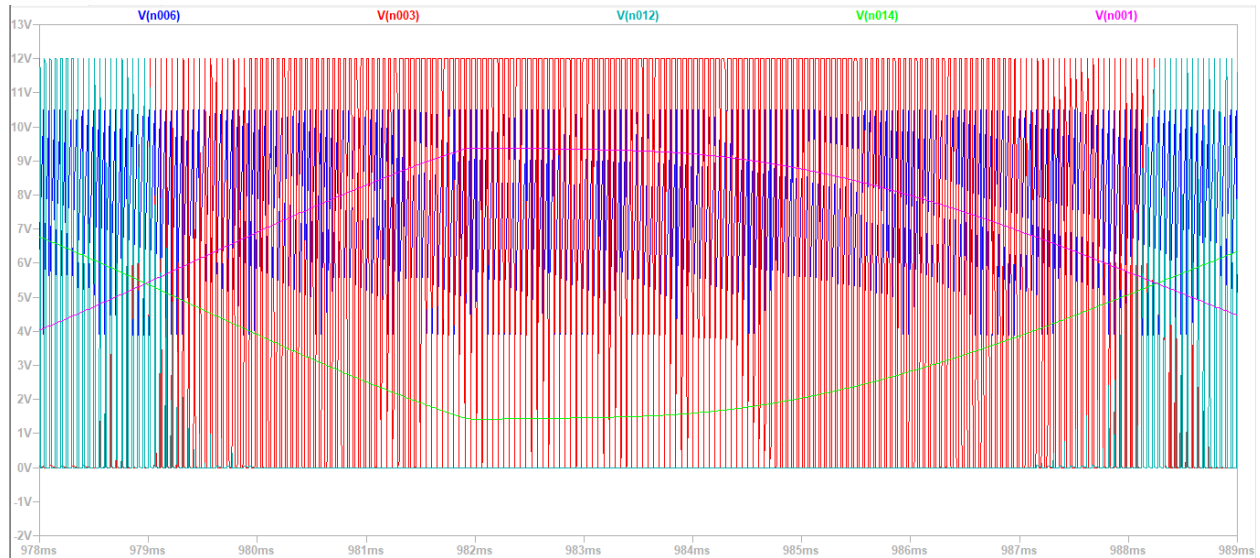


## Hardware model:

### Inverter:

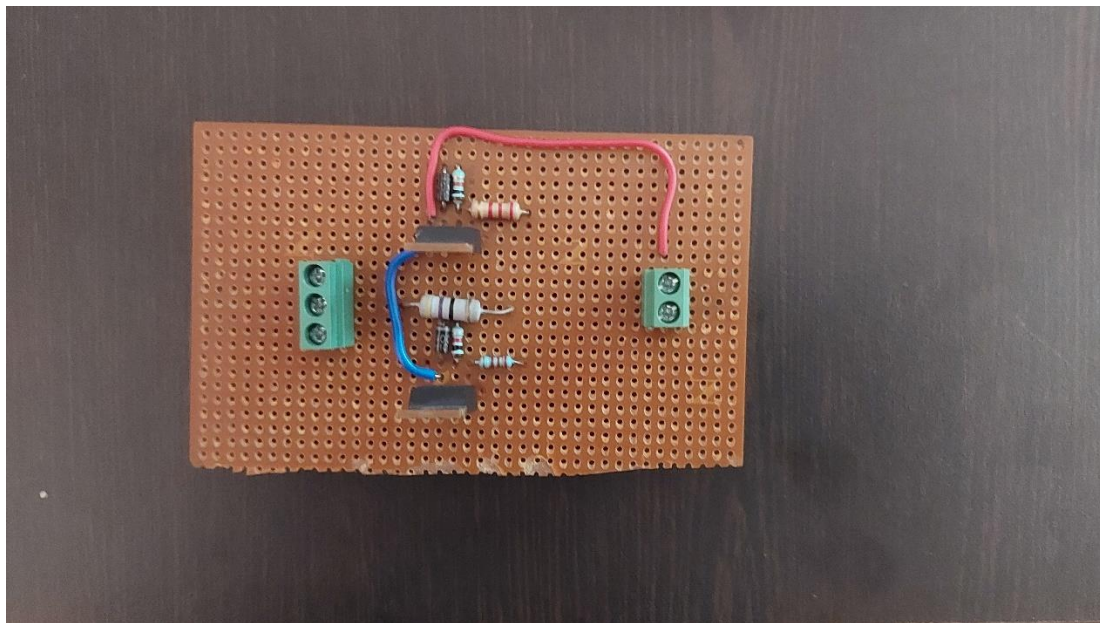





## PWM Circuit:

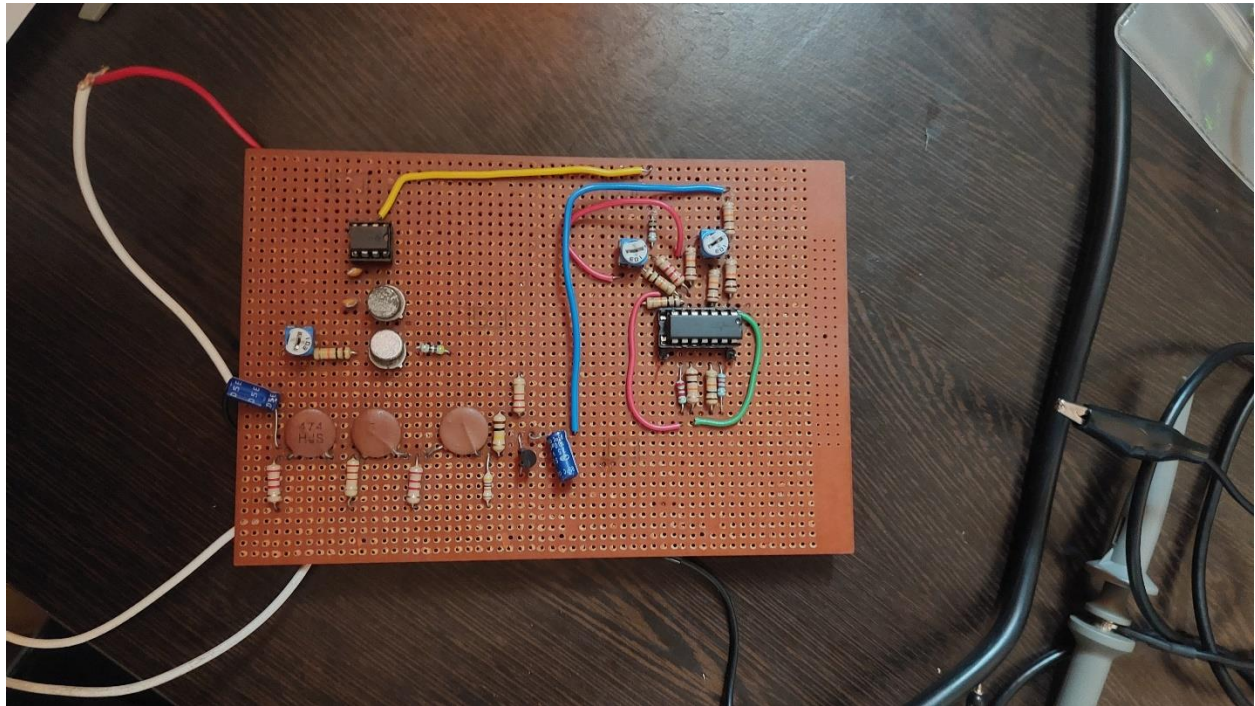

## Hardware output:

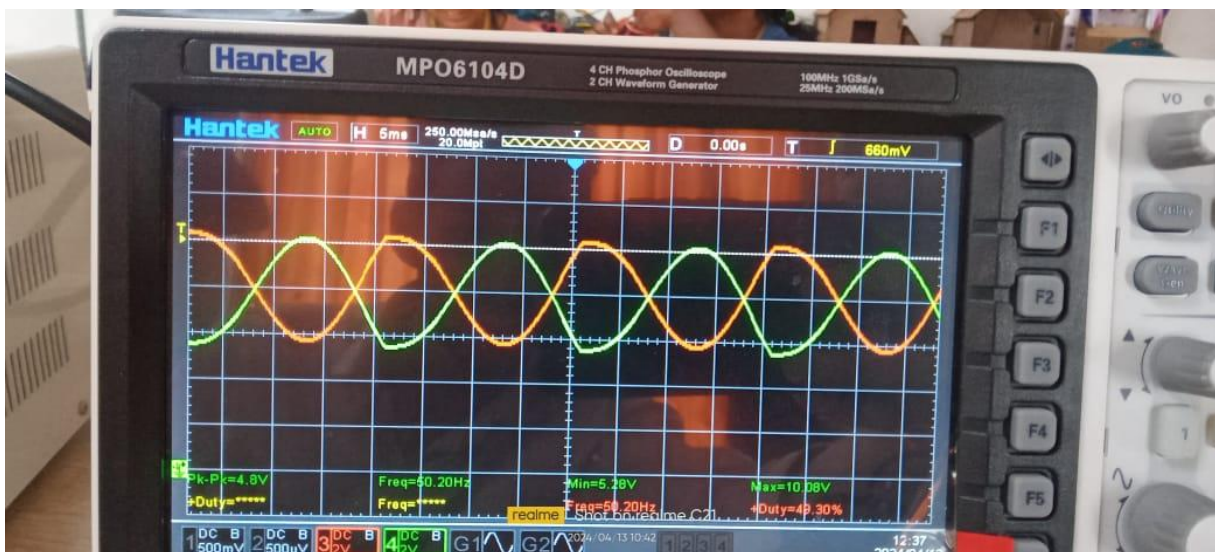

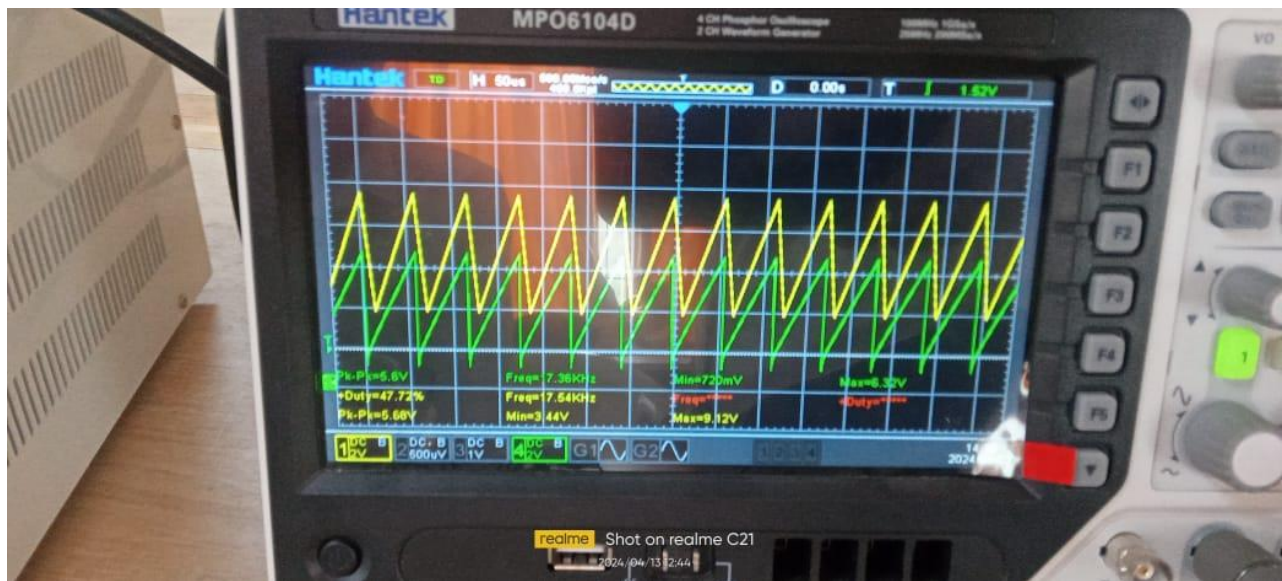

**RESULT:**

**The generated output waveform closely matches the desired output.**